

B.TECH.
(SEM IV) THEORY EXAMINATION 2018-19
ELECTRONICS ENGINEERING

Time: 3 Hours

Total Marks: 100


Note: Attempt all Sections. If require any missing data; then choose suitably.

SECTION A

1. Attempt *all* questions in brief. 2 x 10 = 20
- If $V_T=26\text{mV}$, $I_O=1\mu\text{A}$, $\eta=1$ and $V_D=0.3\text{V}$ then determine the value of diode current I_D .
 - Enlist at least two differences between DMOSFET and EMOSFET.
 - List the four specifications of unregulated power supply.
 - What are Lissajous figure?
 - What are the necessary blocks in multimeter for measuring AC voltage ?
 - If $\text{CMRR}=40\text{dB}$ and $A_{\text{CM}}=2\text{dB}$ then determine the value of A_D .
 - Give biasing condition of E-B and C-B junction of BJT to operate in an active region.
 - A half wave rectifier is fed from secondary of a transformer whose output voltage is 12.6 V, find out the rectified DC output voltage.
 - What kind of resistances are present in a diode?
 - Draw the PIN diagram of IC 741.

SECTION B

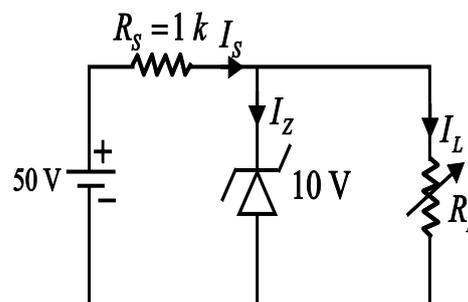2. Attempt any *three* of the following: 10 x 3 = 30
- Explain the working of Digital Voltmeter and Digital Multi Meter giving their block diagram.
 - Explain the formation of depletion region for p-n junction diode. Discuss the effect of biasing and draw its V-I characteristics showing the effect of temperature .
 - Explain Zener diode as a voltage regulator. For the following circuit, determine the range of R_L and I_L such that Zener diode is in breakdown condition. Assume $I_{Z_{\text{max}}} = 32 \text{ mA}$.




- Draw the circuit diagram of Op-Amp as Integrator and Differentiator. Also derive the output voltage expression for both.

- e. An ac supply of 230 V rms is applied to HWR circuit through transformer having turns ratio $\frac{N_1}{N_2} = \frac{4}{1}$. Assume that the diode is ideal and the load resistance is 300 Ω. Find
- (i) DC output voltage.
 - (ii) V_{rms}
 - (iii) PIV
 - (iv) I_{rms} .
 - (v) Maximum value of power delivered to the load.
 - (vi) Average value of power delivered to the load.

SECTION C


3. Attempt any *one* part of the following: 10 x 1 = 10

- (a) Draw and explain the circuit of a full-wave voltage doubler. Also explain briefly the basic function of a filter and also mention its elements.
- (b) Explain the working of n-channel JFET with suitable diagram. Also draw its drain and transfer characteristics. For the given circuit, calculate following parameters:
 (i) V_{GSQ} (ii) I_{DQ} (iii) V_{DS} (iv) V_S (v) V_D (vi) V_G

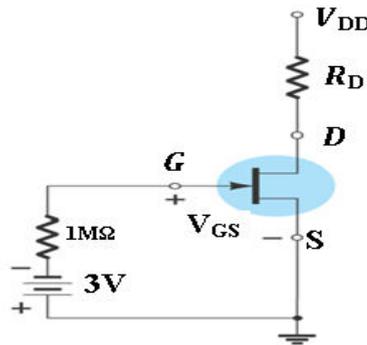

4. Attempt any *one* part of the following: 10 x 1 = 10

- (a) Draw the block diagram of CRO and explain the function of each block. How CRO can be used to measure (i) voltage (ii) frequency (iii) phase difference.
- (b) Assuming silicon transistor in the given circuit, determine:
 (i) I_{BQ} (ii) I_{CQ} (iii) V_{CEQ} (iv) V_E (v) V_C .

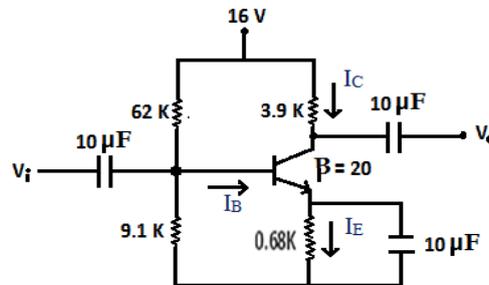


5. Attempt any *one* part of the following: 10 x 1 = 10

- (a) Draw the circuit diagram of difference amplifier using OP-AMP. Derive the expression for its output voltage. Design an inverting amplifier with a gain of -9 and input resistance of 10K ohm.

- (b) Draw the CE configuration circuit of NPN transistor and explain its input and output characteristics. Also derive the stability factor S for the emitter bias configuration.

6. Attempt any *one* part of the following: 10 x 1 = 10

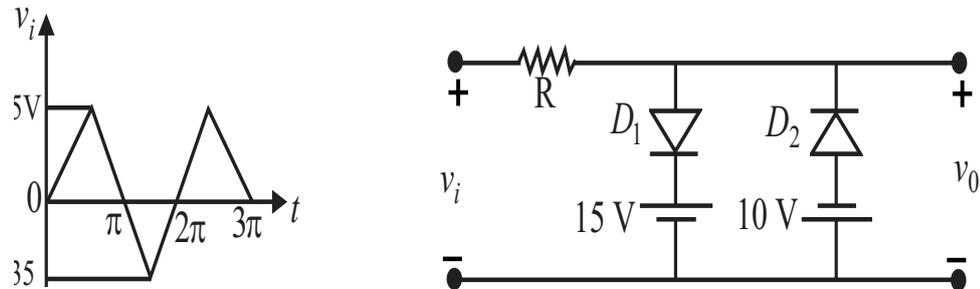- (a) Draw and explain the output waveform for circuit. Assume that the diodes are Si.



- (b) Explain Schottky diode and varactor diode with their applications.

7. Attempt any *one* part of the following: 10 x 1 = 10

- (a) Draw and explain the working of bridge rectifier with input and output waveforms. calculate ripple factor and efficiency.
- (b) Explain following term
- (i) Zero crossing detector using OPAMP
 - (ii) Buffer amplifier (OPAMP)
 - (iii) Slew Rate
 - (iv) CMRR
 - (v) virtual ground condition
 - (vi) mobility